

## Guided Reading in CODE

The reading in **Code** builds up to how we can use binary and transistors to build a computer. Essentially the history of representing information using alternative methods such as Morse code and Braille, were technology breakthroughs. Automating alternative information representations with electricity continued this progress.

Keep reading...

### Chapter 11

1. Briefly describe the four gates explained in Chapter 11. Describe the behavior of each gate based on the input values to the gate.
  - And Gate: in order for a signal to be produced, all switches must be closed. If all n switches are closed, then a signal is produced.
  - OR Gate: Either switch in the circuit can be closed and a signal will be produced. If one switch of n switches is closed, then a signal is produced.
  - NOR Gate: all switches must be open in order to produce a signal. If switch 1 and switch 2 and switch n are open, then a signal will be produced.
  - NAND Gate: if any of n switches are open, then a signal will be produced.

### Chapter 12

2. A half adder is built from how many "sub components" and has how many inputs and outputs?
  - A half adder has two sub-components, two inputs, and two outputs.
3. A full adder is built from how many "sub components" and has how many inputs and outputs?
  - A full adder has 5 components, three inputs, and two outputs.
4. How many total inputs and outputs are there for an 8-bit adding circuit?
  - 17 inputs, including the initial carry in. 9 outputs counting the overflow or carry out.
5. How many total transistors are needed for the ripple version of the 8-bit adder?
  - An eight bit ripple adder uses 144 transistors.